

DESIGN NOTES

L-Network Design Procedure

For maximum power transfer, source and load impedance must have a conjugate match. For many circuits with modest bandwidth requirements, a simple *L-network* comprising two reactive components is the simplest method of achieving that match. This note is a quick review of L-network design.

Figure 1 shows the sequence of steps for matching two impedances, either of which can be considered “source” or “load.” Fig. 1a shows only the resistance of these impedances; their reactances will be dealt with later. Most often, one of the impedances is a common system impedance. For this example, we’ll assume that $R_1 = 50$ ohms, then arbitrarily choose $R_2 = 10$ ohms.

The design process begins with a shunt component (X_p in Fig. 1b) connected in parallel with the higher resistance (R_1). The parallel combination will result in a lower resistance, which we want to be equal to R_2 (10 ohms). Because X_p is reactive, the resulting lower resistance will now have an associated reactance. This is cancelled by the L-network’s series reactance X_s , which is the negative of the reactance introduced by X_p . Thus, the series and shunt components are of opposite reactances—a shunt inductor and a series capacitor, or vice versa.

The design calculation starts by determining circuit Q according to the ratio of the two resistances:

$$Q_s = Q_p = \sqrt{\frac{R_p}{R_s} - 1}$$

where R_p is the resistance adjacent to the parallel leg of the network, and R_s is the resistance at the series-connected end. Q may not be negative, so R_p must be the higher of the two resistances. In our example, $R_1 = R_p$ and $R_2 = R_s$. Note that Q is determined by the source and load, not be user-selected as is typical when designing higher order networks.

The calculation continues as follows:

$$Q_s = \frac{|X_s|}{R_s} \quad \text{or,} \quad |X_s| = Q_s R_s$$

$$Q_p = \frac{R_p}{|X_p|} \quad \text{or,} \quad |X_p| = \frac{R_p}{Q_p}$$

where the reactances are given as magnitude only, since X_s and X_p may be either capacitance or inductance, but as noted above, cannot both be the same.

Applying these equations to our example, we find that $Q = 2$, $|X_s| = 20$ ohms and $|X_p| = 25$ ohms. Before assigning a sign to each reactance, let’s look at

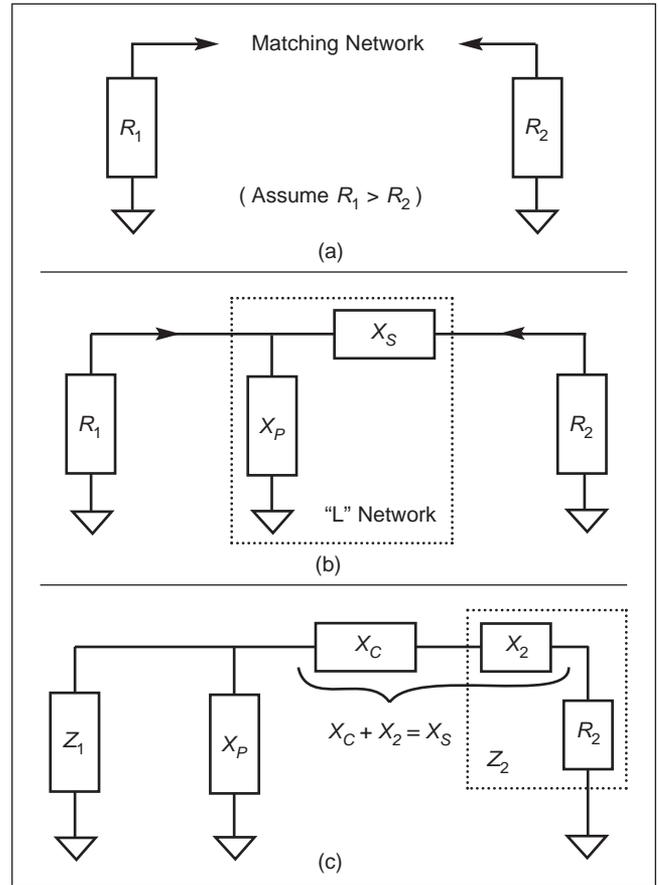


Figure 1 · L-network design sequence.

our example with complex impedances at Z_1 and Z_2 , as in the circuit of Fig. 1c. Since we assumed a system impedance, let $Z_1 = 50 \pm j0$ ohms (same as R_1). Then let’s say that $Z_2 = 10 - j10$ ohms.

In Fig. 1c we see that X_s has been split into two parts: X_2 is the reactive part of Z_2 , and X_c is the final circuit value that makes X_s equal to the sum of X_c and X_2 . We have two choices for the signs of the network reactances, and can examine the effect of each for obtaining practical values of X_c and X_p .

If $X_s = +20$ ohms, then X_c must be +30 ohms. X_p will be -25 ohms.

If $X_s = -20$ ohms, then X_c must be -10 ohms. X_p will be +25 ohms.

One common choice is selecting the configuration to enable or block DC continuity. Let’s say that Z_2 is a transistor output being matched to a 50 ohm transmission line. Since $X_c = -10$ ohms, it is a capacitor and will be useful for blocking DC.

Finally, if Z_1 is complex, X_p would be combined with the reactive portion of Z_1 to compute the actual circuit component value, as was done to find X_c .